

CSCI 355 - Lab Final Report

Student: Luka Karanovic

Student #: 665778833

Instructor: Ajay Shrestha

Priority Encoder

Verilog:

Filename: PriorityEncoder.v

```
module PriorityEncoder(
    input wire [3:0] W,
    output wire [1:0] Y,
    output wire Z
);

    reg [1:0] Y_reg;
    reg Z_reg;

    assign Y = Y_reg;
    assign Z = Z_reg;

    always @(W) begin
        Z_reg = 1'b1;
        casex (W)
            4'b0001: Y_reg = 2'b00;
            4'b001x: Y_reg = 2'b01;
            4'b01xx: Y_reg = 2'b10;
            4'b1xxx: Y_reg = 2'b11;
            default: begin // 0000 case
                Z_reg = 1'b0;
                Y_reg = 2'bxx;
            end
        endcase
    end

endmodule
```

Testbench:

Filename: PriorityEncoder_tb.v

```
module PriorityEncoder_tb();

    reg [3:0] W;
    wire [1:0] Y;
    wire Z;

    PriorityEncoder UT (W, Y, Z);

    initial begin

        W = 4'b0000; #10;
```

```

W = 4'b0001; #10;
W = 4'b0010; #10;
W = 4'b0011; #10;
W = 4'b0100; #10;
W = 4'b0101; #10;
W = 4'b0110; #10;
W = 4'b0111; #10;
W = 4'b1000; #10;
W = 4'b1001; #10;
W = 4'b1010; #10;
W = 4'b1011; #10;
W = 4'b1100; #10;
W = 4'b1101; #10;
W = 4'b1110; #10;
W = 4'b1111; #10;

```

```

$finish;
end

```

endmodule

Waveform:



Moore Modulo-8 Counter

Verilog:

Filename: MooreModulo.v

```

module MooreModulo(
    input wire w, Clk, Resetn,
    output reg [2:0] z
);
    reg [2:0] y, Y; // Current and next state
    // States for current value of output.
    parameter A = 3'b000, B = 3'b001, C = 3'b010, D = 3'b011, E = 3'b100, F = 3'b101, G =
    3'b110, H = 3'b111;

    always @(w, y) begin
        case (y)
            A: if (w) Y = B;

```

```

        else Y = y;
    B: if (w) Y = C;
        else Y = y;
    C: if (w) Y = D;
        else Y = y;
    D: if (w) Y = E;
        else Y = y;
    E: if (w) Y = F;
        else Y = y;
    F: if (w) Y = G;
        else Y = y;
    G: if (w) Y = H;
        else Y = y;
    H: if (w) Y = A;
        else Y = y;
    default: Y = 3'bxxx; // Don't care

endcase
z = y;
end

always @(negedge Resetn, posedge Clk) begin
    #10;

    if (Resetn == 0) y <= A;
    else y <= Y;
end

endmodule

```

Testbench:

Filename: MooreModulo_tb.v

```

module MooreModulo_tb();

    reg Clk = 0;
    reg Resetn = 0;
    reg w;
    wire [2:0] z;

    MooreModulo UT(w, Clk, Resetn, z);

    always begin
        Clk = ~Clk;
        #5;
    end

    initial begin
        w = 0; #20;
    end


```

```

    Resetn = 1;
    w = 1; #60;
    w = 0; #30;
    w = 1; #40;
    w = 1; #20;
    Resetn = 0;
    w = 1; #30;
    w = 0; #20;
    $finish;
end
endmodule


```

Waveform:

 

Mealy

State Diagram:

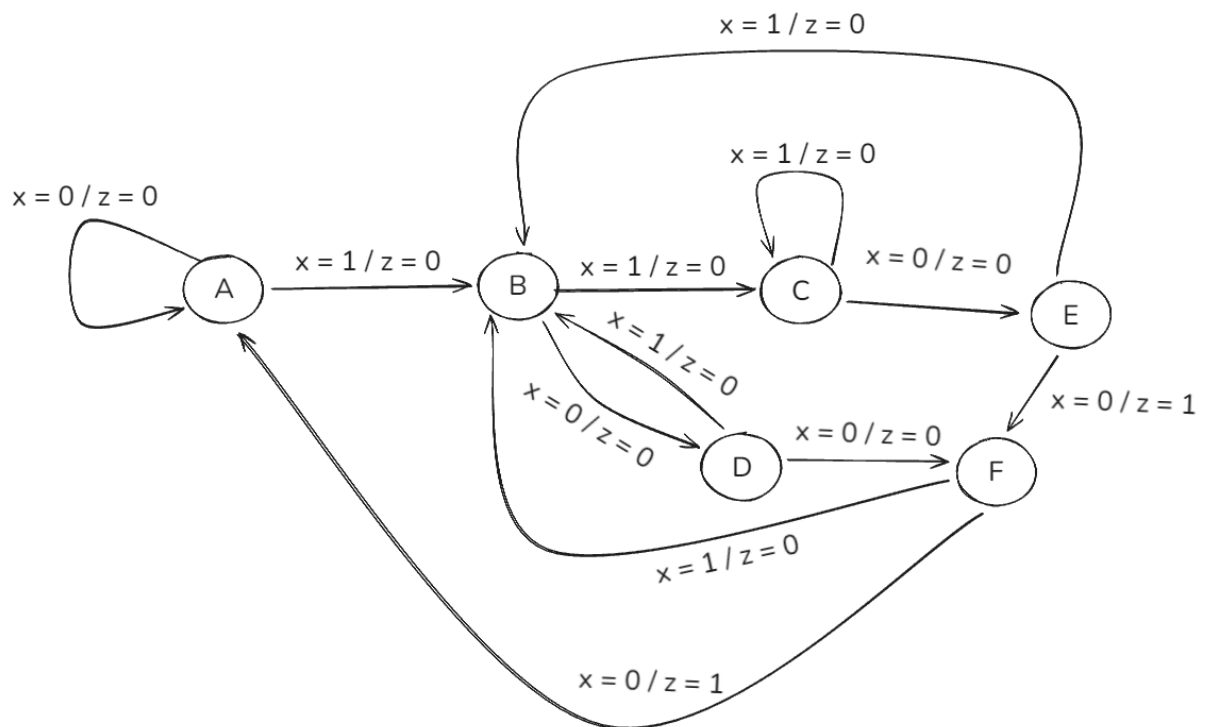

Verilog:

Filename: Mealy.v
 module Mealy(

```
input wire Clk, x,  
output reg z  
);
```

```
reg [2:0] y, Y;  
parameter A = 3'b000, B = 3'b001, C = 3'b010, D = 3'b011, E = 3'b100, F = 3'b101;
```

```
// Determine next state and output z based on input w.
```

```
always @(x, y) begin
```

```
    case (y)
```

```
        A: if (x) begin
```

```
            Y = B;
```

```
            z = 0;
```

```
        end
```

```
        else begin
```

```
            Y = A;
```

```
            z = 0;
```

```
        end
```

```
        B: if (x) begin
```

```
            Y = C;
```

```
            z = 0;
```

```
        end
```

```
        else begin
```

```
            Y = D;
```

```
            z = 0;
```

```
        end
```

```
        C: if (x) begin
```

```
            Y = C;
```

```
            z = 0;
```

```
        end
```

```
        else begin
```

```
            Y = E;
```

```
            z = 0;
```

```
        end
```

```
        D: if (x) begin
```

```
            Y = B;
```

```
            z = 0;
```

```
        end
```

```
        else begin
```

```
            Y = F;
```

```
            z = 0;
```

```
        end
```

```
        E: if (x) begin
```

```
            Y = B;
```

```
            z = 0;
```

```
        end
```

```
        else begin
```

```
            Y = F;
```

```

        z = 1;
    end
    F: if (x) begin
        Y = B;
        z = 0;
    end
    else begin
        Y = A;
        z = 1;
    end
    default: Y = A; // If no current state, set next state to initial state
endcase
end

// Handle clock updates and reset, reset is async and happens when it is set to 0.
always @(posedge Clk) begin
    #10;
    y <= Y;
end

endmodule

```

Testbench:

Filename: Mealy_tb.v

```

module Mealy_tb();
    reg Clk = 0;
    reg x;
    wire z;

    Mealy UT(Clk, x, z);

    always begin
        Clk = ~Clk;
        #5;
    end

    initial begin
        x = 0; #10;
        x = 0; #10;
        x = 1; #10;
        x = 1; #10;
        x = 0; #10;
        x = 0; #10;
        x = 0; #10;
    end

```


```

x = 1; #10;
x = 0; #10;
x = 1; #10;
x = 1; #10;
x = 0; #10;
x = 0; #10;
x = 1; #10;
x = 0; #10;
x = 0; #10;
x = 0; #10;
x = 1; #10;
x = 0; #10;
x = 1; #10;
x = 0; #10;
x = 1; #10;
x = 1; #10;
x = 0; #10;
x = 0; #10;
$finish;
end

```

endmodule

Waveform:

 

Serial Adder FSM

Verilog:

Filename: serialAdder.v

```

module shiftReg #(parameter n = 8)
(
    input Clk,           // Pos-edge clock
    input wire E,        // Enable signal
    input wire L,        // Load
    input wire [n-1:0] pdata, // Parallel data
    input wire w,        // Serial data
    output reg [n-1:0] Y // Output
);
    integer i;
    always @(posedge Clk) begin
        if (E) begin
            if (L) begin // Parallel load
                Y <= pdata;
            end
        end
    end
endmodule

```



```

        end
        else begin // Serial load
            for (i = 0; i < n-1; i = i+1) begin
                Y[i] <= Y[i+1];
            end
            Y[n-1] <= w;
        end
        // Else: E is 0 and Y holds its value
    end
endmodule

```

```

module serialAdder(
    input Clk,           // Pos-edge clock
    input wire Reset,    // Enable signal
    input wire [7:0] A,  // Input data A
    input wire [7:0] B,  // Input data B
    output wire [7:0] S  // Sum
);
    wire a, b;           // Serial output from shift regs
    reg E;               // Enable for sum shift reg
    reg s;               // Serial sum input to sum shift reg
    reg Cin = 0, Cout;   // Current and next state for Adder FSM
    reg [3:0] counter = 4'b1000; // Counter initialized to 1000 like diagram
    parameter G = 1'b0, H = 1'b1; // Possible states (Cin and Cout values)

    shiftReg shiftA(Clk, 1, Reset, A, 0, a);
    shiftReg shiftB(Clk, 1, Reset, B, 0, b);
    shiftReg shiftS(Clk, E, Reset, 0, s, S);

    // Mealy Adder FSM
    always @(a, b, Cin) begin
        case (Cin)
            G: if (a ^ b) begin // ab = 10 or 01
                s = 1;
                Cout = G;
            end
            else if (a && b) begin // ab = 11
                s = 0;
                Cout = H;
            end
            else begin // ab = 00
                s = 0;
                Cout = G;
            end
        end
        H: if (a ^ b) begin // ab = 10 or 01
            s = 0;
            Cout = H;
        end
    end
endmodule

```

```

        end
        else if (a && b) begin // ab = 11
            s = 1;
            Cout = H;
        end
        else begin // ab = 00
            s = 1;
            Cout = G;
        end
        default: Cout = G; // If nothing, Cout is 0

    endcase
end

always @(posedge Clk, Reset) begin
    #10;
    Cin <= Cout;
    if (!counter) begin // If there is a 1 in counter
        E = 1;
        counter = counter + 1;

    end
    else begin // Low E signal after one n-bit addition.
        E = 0;
    end

    if (Reset) begin
        counter = 4'b1000;
        Cin <= 0;
    end
end

endmodule

```

Testbench:

Filename: serialAdder_tb.v

```
module serialAdder_tb();
```

```

    reg Clk = 0;
    reg Reset = 1;
    reg [7:0] A, B;

```

```
    wire [7:0] S;
```

```
    serialAdder UT(Clk, Reset, A, B, S);
```

```
always begin
```

```
    Clk = ~Clk;
```

```
    #5;
```

```
end
```

```
initial begin
```

```
    A = 8'hA4;
```

```
    B = 8'h2D;
```

```
    #15; // So things can load
```

```
    Reset = 0; #120;
```

```
    $finish;
```

```
end
```

```
endmodule
```

Waveform:

