

CSCI 355 - Lab 4 Report

Student: Luka Karanovic

Student #: 665778833


Instructor: Ajay Shrestha

1 - Pre-Lab Answers

Note: All K-map grouping are circled in blue. All distinguished cells are circled in red.


4.1 - Using Karnaugh maps, find minimal sum-of-products expressions for the following logic functions. Indicate the distinguished 1-cells in each one that you do.

 a) $F = \sim XY\sim Z + X\sim Z + XY + XZ + \sim YZ$



Minimum-cost SOP is $F = \sim YZ + Y\sim Z + X$

 
b) $F = X\sim Y + W\sim Y + X\sim Z + W\sim Z + \sim YZ + \sim WX$



Minimum-cost SOP is $F = \sim YZ + \sim WX + X\sim Z$


4.2 - Using Karnaugh maps, find minimal product-of-sums expressions for the following logic functions. Indicate the distinguished 0-cells in each one that you do.

 a) $F = \prod W, X, Y, Z(0, 1, 8, 9, 10, 12, 14)$



Minimum-cost POS is $F = (\bar{W} + Z)(X + Y)$

b) $F = \Pi W, X, Y, Z(0, 15)$

 


Minimum-cost POS is $F = (W + X + Y + Z)(\bar{W} + \bar{X} + \bar{Y} + \bar{Z})$

 4.3 Find a minimal sum of products expression for the following logic function using a 5-variable K-map.

$$F = \sum_{V,W,X,Y,Z} (0,7,8,9,12,13,15,16,22,23,30,31)$$


Orange circles and dotted lines mean that the prime implicants are connected between boards (V doesn't matter).



Minimum-cost SOP is $F = (\sim V W \sim Y) + (X Y Z) + (\sim W \sim X \sim Y \sim Z) + (V X Y)$

 
4.4 K-map "Don't Care"s

- Using Karnaugh maps, find a minimal sum-of-products expression for a BCD evenly divisible-by-3 detector NOT using don't-cares, represented by $F = \sum W, X, Y, Z m(0,3,6,9)$



Minimum-cost SOP not using don't-cares is $F = (\sim W \sim X \sim Y \sim Z) + (\sim W \sim X Y Z) + (W \sim X \sim Y Z) + (\sim W X Y \sim Z)$

 - b) Using Karnaugh maps, find a minimal sum-of-products expression for a BCD evenly divisible-by-3 detector using don't-cares, represented by $F = \Sigma W, X, Y, Z m(0,3,6,9) + \Sigma D(10,11,12,13,14,15)$.



Minimum-cost SOP using don't-cares is $F = (\sim W \sim X \sim Y \sim Z) + (\sim X Y Z) + (X Y \sim Z) + (W Z)$

2 - Lab Procedures

6.1 Three-Way Light Control using structural Verilog

i) Write the structural (i.e., using gate primitives) Verilog HDL code for a three-way light control (see Section 3.2) with the module interface as shown below, implemented as a sum-of-products. Simulate in the Vivado with testbench to verify operation.

The SOP is the three-way light control is: $f = (\sim x_1 + \sim x_2 + x_3)(\sim x_1 + x_2 + \sim x_3)(x_1 + \sim x_2 + \sim x_3)(x_1 + x_2 + x_3)$

ii) You should include a Verilog main code, testbench, and picture of the timing diagram in your lab report

Filename: ThreeWayLight_structural.v

```
module ThreeWayLight_structural(x1, x2, x3, light);
    input x1, x2, x3;
    output light;

    wire w1, w2, w3, w4, n1, n2, n3;

    not(n1, x1);
    not(n2, x2);
    not(n3, x3);

    or(w1, n1, n2, x3);
    or(w2, n1, x2, n3);
```

```

        or(w3, x1, n2, n3);
        or(w4, x1, x2, x3);

        and(f, w1, w2, w3, w4);
    endmodule

```

Filename: threewaylight_tb.v

```

module threewaylight_tb();


    reg a, b, c;
    wire f;
    ThreeWayLight_structural vt(a, b, c, f);
    ThreeWayLight_behavioural ut(a, b, c, f);

    initial begin
        {a,b,c} = 3'd0; #20;
        {a,b,c} = 3'd1; #20;
        {a,b,c} = 3'd2; #20;
        {a,b,c} = 3'd3; #20;
        {a,b,c} = 3'd4; #20;
        {a,b,c} = 3'd5; #20;
        {a,b,c} = 3'd6; #20;
        {a,b,c} = 3'd7; #20;
        $display("Done");
        $finish;
    end

endmodule

```

Waveform (used same testbench for both):

 

iii) Fill out the truth table with the result from the timing diagram and comment if the waveform is as expected.

x1	x2	x3	f
0	0	0	0
0	0	1	1
0	1	0	1

0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Waveform is working as expected.

6.2 Three-Way Light Control using behavioural Verilog

ii) You should include a Verilog main code, testbench, and picture of the timing diagram in your lab report

Filename: ThreeWayLight_behavioural.v

```
module ThreeWayLight_behavioural(x1, x2, x3, light);
```

```
    input x1, x2, x3;
    output light;
```

```
    wire w1, w2, w3, w4, n1, n2, n3;
```

```
    assign n1 = ~x1;
    assign n2 = ~x2;
    assign n3 = ~x3;
```

```
    assign w1 = (x1 | n2 | n3);
    assign w2 = (n1 | x2 | n3);
    assign w3 = (n1 | n2 | x3);
    assign w4 = (x1 | x2 | x3);
```

```
    assign light = (w1 & w2 & w3 & w4);
```

```
endmodule
```

Note: you could do the entire SOP in one line but I think this is more readable.

Filename: threewaylight_tb.v

```
module threewaylight_tb();
```

```
    reg a, b, c;
    wire f;
    ThreeWayLight_structural vt(a, b, c, f);
    ThreeWayLight_behavioural ut(a, b, c, f);
```


```
    initial begin
        {a,b,c} = 3'd0; #20;
```

```

{a,b,c} = 3'd1; #20;
{a,b,c} = 3'd2; #20;
{a,b,c} = 3'd3; #20;
{a,b,c} = 3'd4; #20;
{a,b,c} = 3'd5; #20;
{a,b,c} = 3'd6; #20;
{a,b,c} = 3'd7; #20;
$display("Done");
$finish;
end
endmodule

```

Waveform (used same testbench for both):

 

iii) Fill out the truth table with the result from the timing diagram and comment if the waveform is as expected.

x1	x2	x3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Waveform is working as expected.